

Sixth Semester B.Sc. Degree Examination, April/May 2019*(Revised CBCS – 2018 Onwards)***Physics****Paper VII — EMBEDDED SYSTEM : INTRODUCTION TO MICROCONTROLLERS OP-AMP AND QUANTUM MECHANICS***Time : 3 Hours]**[Max. Marks : 90**Instructions to Candidates : Answers should be written completely in English.***PART – A**

- I. Answer any **FIVE** of the following. Each question carries **8** marks. **(5 × 8 = 40)**
1. (a) What is an operational amplifier?
(b) Explain with circuit how an op-amp functions as an non-inverting amplifier. **(1 + 7)**
 2. (a) Mention the characteristics of an ideal op-amp.
(b) Explain how op-amp can be used as a differentiator. Also derive an expression for its output. **(4 + 4)**
 3. With a neat circuit diagram, explain the working of a phase shift oscillator. What are its disadvantages? **(8)**
 4. Describe the internal architecture of the 8051 with schematic diagram. **(8)**
 5. (a) List out the features of the 8051 microcontroller.
(b) Discuss the function of various flags in PSW register. **(4 + 4)**
 6. Explain the pin diagram of the 8051 micro controller. **(8)**
 7. (a) Give the physical significance of a wave function.
(b) Obtain the expression for the Schrodinger time dependent equation. **(2 + 6)**
 8. Derive an expression for the time independent Schrodinger equation. **(8)**

PART – B

- II. Answer any **SIX** of the following. Each question carries **5** marks. **(6 × 5 = 30)**
9. In the subtractor circuit $R_1 = 5k\Omega$, $R_f = 10k\Omega$, $V_1 = 4V$ and $V_2 = 5V$. Find the value of the output voltage. V_1 and V_2 are potentials at the non-inverting and inverting terminals respectively.
 10. Determine the output voltage of a differential amplifier for the input voltage of $300 \mu v$ and $240 \mu v$. The differential gain of the amplifier is 5000 and the value of CMRR is 100.
 11. An amplifier with negative feedback has a voltage gain of 100. It is found that without feedback, an input signal of 50 mV is required to produce a given output, whereas with feedback the input signal must be 0.6 V for the same output, calculate the value of A and B.
 12. Write a program to add 25 H, 34 H and 12 H using 8051 assembly language.
 13. Write a program to multiply two 8 bit numbers stored at location 70 H and 71 H and store the result at memory locations 52 H and 53 H.
 14. Find the probability that a particle in one dimensional box of length L can be found 0.4 L to 0.8 L for the ground state. Given $\psi = \left(\frac{2}{L}\right)^{\frac{1}{2}} \sin\left(\frac{n\pi x}{L}\right)$.
 15. A particle limited to the x-axis has the wave function $\psi = ax$ between $x = 0$ and $x = 1$, $\psi = 0$, elsewhere. Find the expectation value of the particle position.
 16. The position and momentum of a 1.1 KcV electron are simultaneously determined. If its position is located within $1A^0$, what is the percentage of uncertainty in its momentum.

PART – C

- III. Answer any **TEN** of the following. Each question carries **2** marks. **(10 × 2 = 20)**
17. (a) Write any two merits of integrated circuit technology.
(b) What are monolithic integrated circuits?

Q.P. Code – 42631

- (c) What happens to the input and output impedance in a voltage series feedback?
 - (d) What is meant by open loop gain of an op-amp?
 - (e) Mention any two applications of a microcontroller.
 - (f) Why microprocessor is faster than microcontroller?
 - (g) What are the size of RAM and ROM memory of 8051?
 - (h) Name any two 16 bit register in the 8051.
 - (i) What are eigen values and eigen functions?
 - (j) Write the expressions for momentum and energy operators.
 - (k) Distinguish between a free particle and particle in a box.
 - (l) The concept of trajectory has no meaning in quantum mechanics. Explain.
-